

Lesson EPSI-03-01 Download the pdf file

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE

- EPSI-03-01: recorded live, Dec 1, 2013
 - The root cause of reflection noise and how to reduce it
 - Download a copy of the slides



Teledyne LeCroy Signal Integrity Academy

1

Lesson EPSI-03-10 How to Think About Reflections

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE

- EPSI-03-10: recorded live, Dec 1, 2013
 - Uniform lines and propagating signals
 - Reflection and transmission coefficients
 - The impact of reflections
 - It's all about what happens at one interface




Teledyne LeCroy Signal Integrity Academy

2


EPSI: A 2-Day Workshop

- **Day 1**
 - EPSI 1 Transmission Lines
 - EPSI 2 Differential Pairs and Lossy Lines
 - Lunch
 - EPSI 3 Reflections and Terminations
 - EPSI 4 Routing Topologies and Discontinuities
- **Day 2**
 - EPSI 5 Eliminating Ground Bounce
 - EPSI 6 Navigating Return Path Discontinuities
 - Lunch
 - EPSI 7 NEXT and FEXT Features
 - EPSI 8 PDN and EMI Design

 Essential Principle# 5: Signals Will Reflect Whenever The Instantaneous Impedance Changes




 If the instantaneous impedance is constant, the signal continues undistorted.



Ringing is caused by multiple reflections from impedance discontinuities at both ends of a line

 If the instantaneous impedance changes, some of the signal reflects.




V_{incident}

$V_{\text{transmitted}}$


$$t = \frac{V_t}{V_i} = \frac{2 \times Z_2}{Z_2 + Z_1}$$

$V_{\text{reflected}}$
 
$$\rho = \text{rho} = \frac{V_r}{V_i} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$



 Multiple sources of impedance discontinuities will create reflections that can rattle around and can dramatically distort the signal



Lesson EPSI-03-20 Voltage and Current Reflections

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE


- EPSI-03-20: recorded live, Dec 1, 2013
 - Reflections from opens and shorts
 - What happens to the current in reflections
 - The bounce diagram and keeping track of reflections
 - Why simulation is essential



Teledyne LeCroy Signal Integrity Academy

5

 
Exercise The Essential Principles: Reflections at an Open or Short



$$\rho = \text{rho} = \frac{V_r}{V_i} = \frac{\infty - Z_1}{\infty + Z_1} = 1$$

 $I_{\text{incident(cw)}}$ $I_{\text{reflected(ccw)}}$

Net current is 0- it's an open!

 

$$\rho = \text{rho} = \frac{V_r}{V_i} = \frac{0 - Z_1}{0 + Z_1} = -1$$

 $I_{\text{incident(cw)}}$ $I_{\text{reflected(cw)}}$





Net current is twice- they add



Teledyne LeCroy Signal Integrity Academy

6

Predicting Reflection Noise

    

Single Bit Response (SBR)
Circuit simulation is critical to evaluate acceptable designs:
SPICE, QUCS, HyperLynx...
Rules of thumb, approximations are not good enough.
ALL the details matter, some more than others

Lesson EPSI-03-30 Practice safe simulation

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE


- EPSI-03-30: recorded live, Dec 1, 2013
 - Rule #9: How to practice safe simulation
 - A free simulation tool included in the downloaded .zip folder
 - Why it takes 2 reflections to cause problems
 - Impact on reflected and transmitted signal from all the parameters

Practice Safe Simulation

Rule #9: Never do a measurement or simulation without first anticipating what you expect to see.

- If you are wrong, there is a reason- either the set up is wrong or your intuition is wrong. Either way, by exploring the difference, you will learn something
- If you are right, you get a nice warm feeling that you understand what is going on.

Dynamic Simulation of Reflected Signals

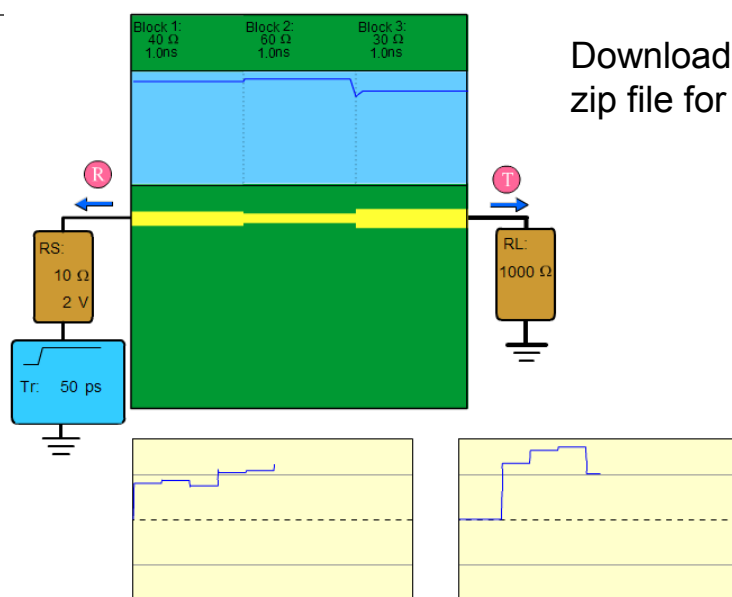

Download this free animation tool in the zip file for this lesson

VScale x 1 R Reflected Waveform VScale x 1 T Transmitted Waveform

Lesson EPSI-03-40 Noise margins

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE


- EPSI-03-40: recorded live, Dec 1, 2013
 - The problem with reflections
 - Noise margins and timing jitter
 - Reflections and inter symbol interference (ISI)
 - Solving reflection problems



Teledyne LeCroy Signal Integrity Academy

11

Acceptable Performance: Noise Margins

 

	VOH	VIH	Margin	VIL	VOL	Margin
TTL [5volt]	2.4V	2.0V	400mV	0.8v	0.5v	300mV
FCT [5volt]	2.5V	2.0V	500mV	0.8v	0.5v	300mV
BTL [5 volt]	2.1V	1.62V	480mV	1.47v	1.1v	370mV
GTL [5 volt]	1.5V	1.05V	450mV	0.95v	0.55v	400mV
CMOS [5 volt]	4.9V	3.85V	1050mV	1.35v	0.1	1340mV
LVTTTL [3volt]	2.4V	2.0V	400mV	0.8v	0.4v	400mV
LVC MOS [3 volt]	2.8V	2.0V	800mV	0.8v	0.2v	600mV
CMOS [2.5V]	2.0V	1.7V	300mV	0.7v	0.4v	300mV
CMOS [1.8V]	1.35V	1.1V	250mV	0.66v	0.45v	210mV

For 5 V CMOS, noise margin-hi/lo ~ 1/5 ~ 20%
 For 2.5 V CMOS, noise margin-hi/lo ~ 0.3/2 ~ 15%
 For 1.8 V CMOS, noise margin-hi/lo ~ 0.25/1.35 ~ 18%

Typical noise margin for single-ended CMOS technology ~ 15% of signal swing


Noise budget allocation: ~ 1/3 to reflection noise, ~1/3 to xtk, ~1/3 to PDN noise



Teledyne LeCroy Signal Integrity Academy


12

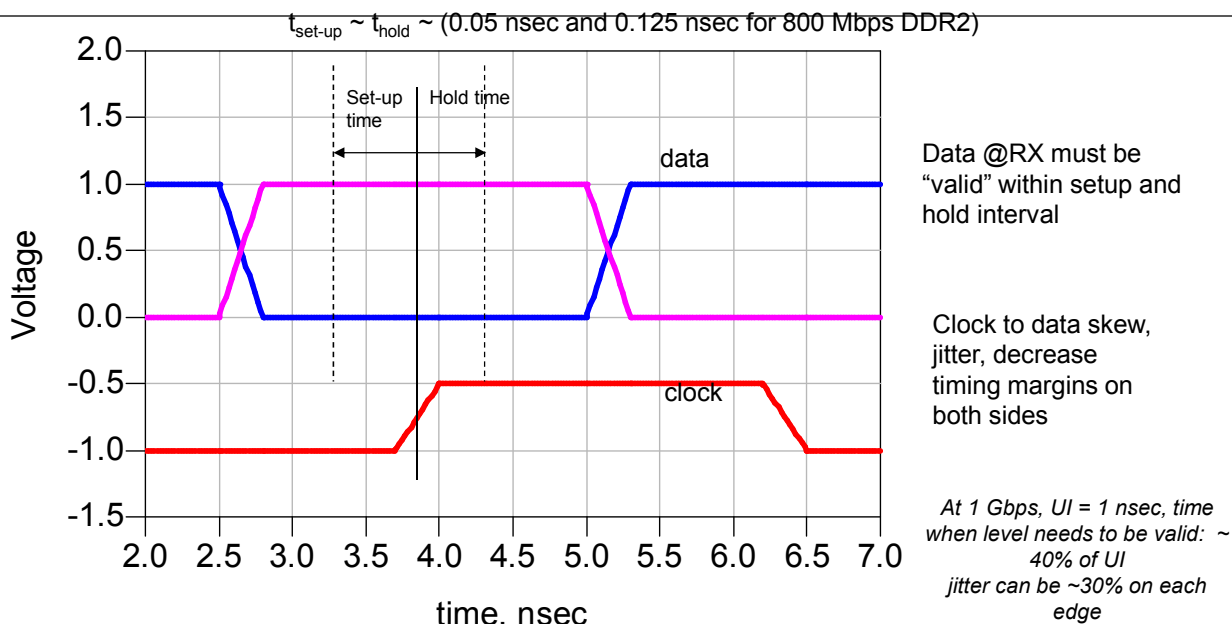Acceptable Performance: Timing Margin for "Valid" Level




The Eye Diagram: The Most Important FINAL Metric of Performance

 A Pseudo Random Bit Sequence (PRBS)
(all possible combinations of bit patterns)



A synchronous clock
2 bits per clock (double data rate)
Data read edge-triggered

 Take every 2 bits,
Align synchronous with the clock
Superimpose: The Eye Diagram





If ALL RX voltage is outside the mask, bit error rate will be acceptable

If any signal "violates" the mask, there may be a bit error

Vertical collapse: noise margin (noise)
Horizontal collapse: timing margin (jitter)

The Problem: Mask Violations (collapse of the eye)

@ 2.5 Gbps

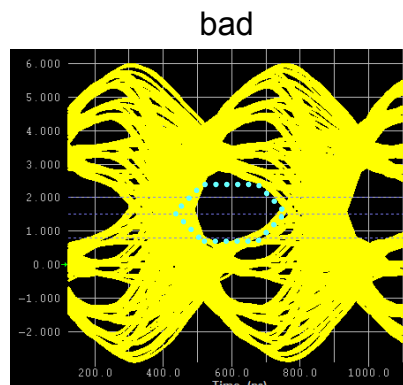 

- The process to “get it right the 1st time”:
 - Identify the problem: collapse of the eye
 - Find the root cause: why do eyes go bad?
 - Turn root cause into practical design guidelines
 - Understand the “essential principles” of how physical design affects signal performance
 - Evaluate tradeoffs with analysis tools as early in the design process as possible

Lesson EPSI-03-50 Four sources of reflections


Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE

- EPSI-03-50: recorded live, Dec 1, 2013
 - Applying the Youngman Principle to reduce reflection noise
 - The four sources of reflection noise
 - Non-uniform lines, ends, routing topology, discontinuities
 - Uniform transmission lines and 2D field solvers


Applying the Youngman Principle: Turn root cause into best design practices

- Reflections can cause signal distortion and collapse of the eye.
- If the root cause of reflections is changes in the instantaneous impedance, what general guideline do we follow to eliminate reflection noise?
 - Keep the instantaneous impedance the signal sees constant
- Four typical situations to engineer:
 1. Problem: non-uniformity of the transmission lines
 - *Solution: use controlled impedance lines*
 2. Problem: the ends of the lines
 - *Solution: use a termination strategy*
 3. Problem: routing topology
 - *Solution: use a linear route, keep branches short*
 4. Problem: discontinuities
 - *Solution: keep them short, match to line impedance*

 


Practical Design Guideline: 1. Use Controlled Impedance Lines

 - Example: four different uniform segments: 40 Ω - 60 Ω



 - Solution: Adjust cross section of each segment to hit target impedance (use 2D field solver)



Lesson EPSI-03-60 Termination topologies

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE


- EPSI-03-60: recorded live, Dec 1, 2013
 - Terminations to prevent reflections
 - Source series terminations
 - Far end termination
 - What's the problem with far end terminations





Teledyne LeCroy Signal Integrity Academy

19

 Practical Design Guideline: Two General Termination Strategies





No termination

  



Far end parallel
termination

$$R_{\text{term}} = Z_0$$

  

Source series termination
  
$$R_{\text{source}} = Z_0 - Z_{\text{driver}}$$



For point to point, all have equivalent signal quality




Teledyne LeCroy Signal Integrity Academy

20

Two Important Properties of EVERY Driver: Rise Time, Output Impedance


10-90 Rise Time
Output impedance

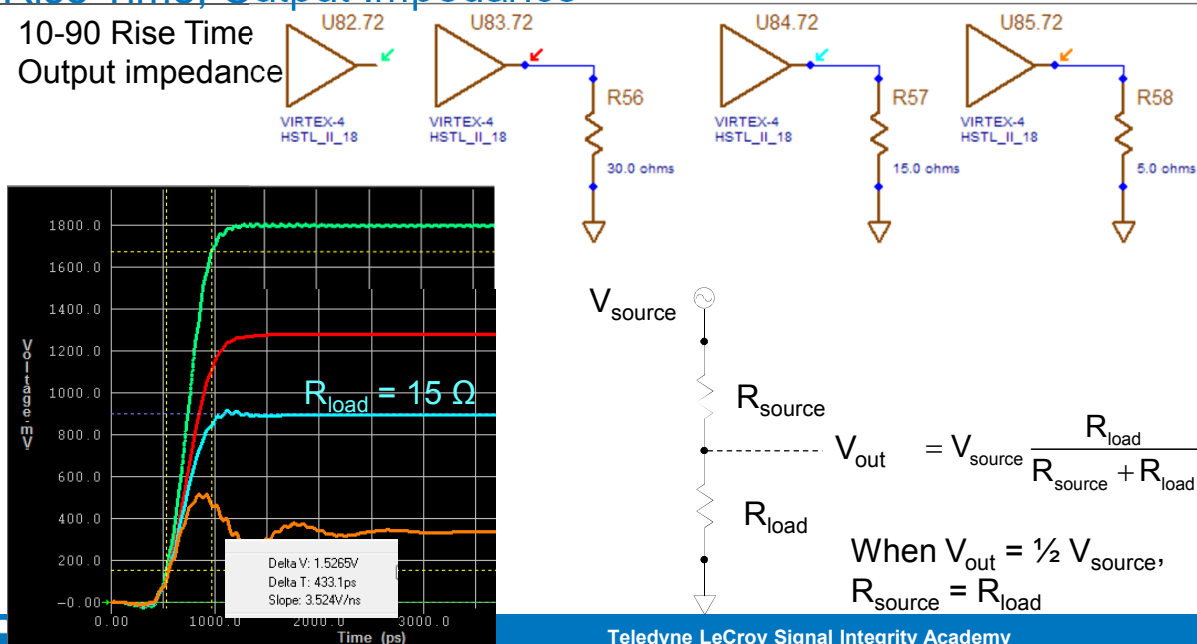

Teledyne LeCroy Signal Integrity Academy

21

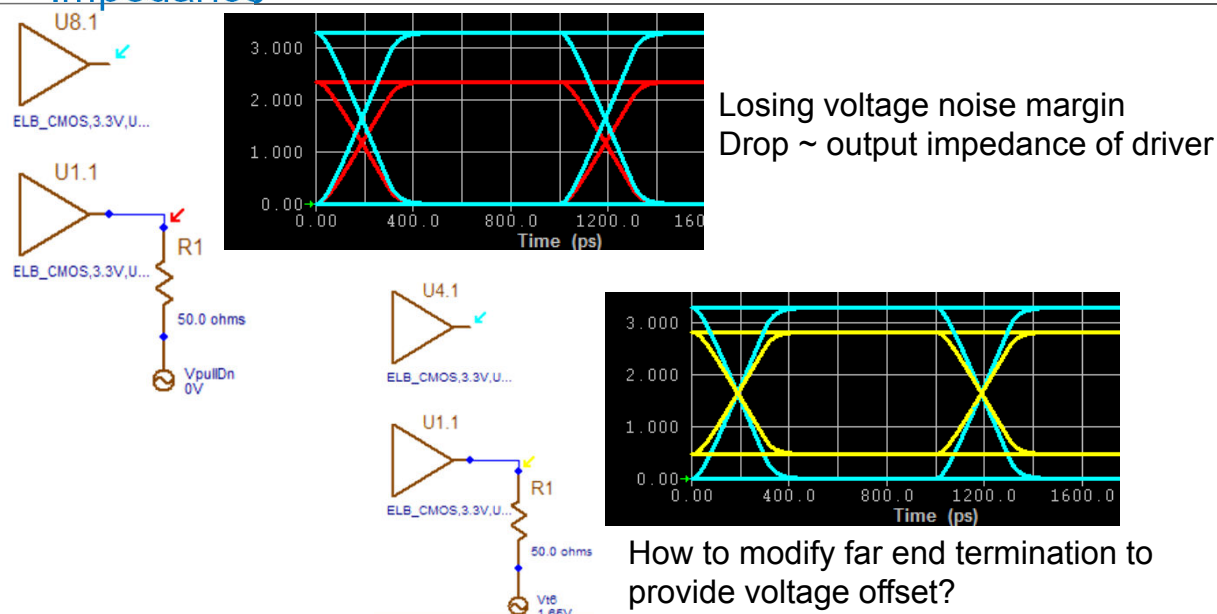Decision #1: Received Signal Swing Due to Finite Output Impedance



TELEDYNE LECROY
Everywhere you look

Teledyne LeCroy Signal Integrity Academy

22

Lesson EPSI-03-70 Balancing Power and Signal Quality

Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE



- EPSI-03-70: recorded live, Dec 1, 2013
 - RC, thevenin and Vtt termination
 - Estimating power dissipation in different terminations
 - Surprising differences in power dissipation
 - Limitations with RC terminations and why clocks are best



Teledyne LeCroy Signal Integrity Academy

23

 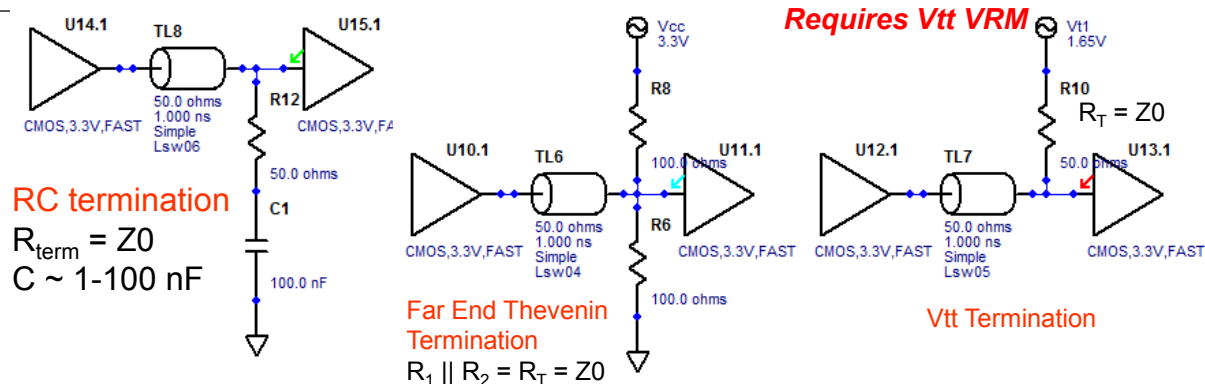Three Other Variations of Far End Termination



For point to point, all have equivalent signal quality.

Key feature of these approaches: centers signal about $\frac{1}{2} V_{CC}$

How do we decide which ones to use, when?




Teledyne LeCroy Signal Integrity Academy

24


Decision #2: Power Consumption

- Power is consumed in resistors:
 
$$\langle P \rangle = \frac{1}{2} \left(\frac{\Delta V_{lo}^2}{R} + \frac{\Delta V_{hi}^2}{R} \right) \quad \langle P \rangle = \frac{1}{2} (I_{lo}^2 R + I_{hi}^2 R)$$




 *Can be very low power dissipation.
If you live for low power, source series
termination should be your first choice*




Power consumed by far end termination (50% duty cycle) =
 
$$\langle P \rangle = \frac{1}{2} \left(\frac{0^2}{50} + \frac{3.3^2}{50} \right) = 100\text{mW}$$



*Much less power if << 50% duty cycle, or >> 50% duty
cycle and Vcc termination*

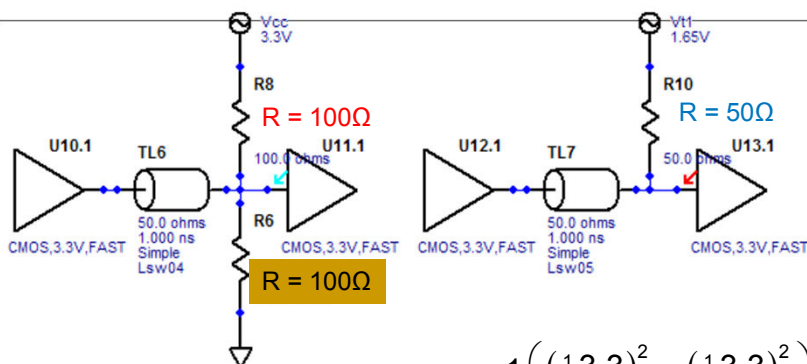Power Consumed in Other Far End Terminations




$$\langle P \rangle = \frac{1}{2} \left(\frac{\Delta V_{lo}^2}{R} + \frac{\Delta V_{hi}^2}{R} \right)$$




$$\langle P \rangle = \frac{1}{2} \left(\frac{\left(\frac{1}{2} 3.3\right)^2}{50} + \frac{\left(\frac{1}{2} 3.3\right)^2}{50} \right) = 50\text{mW}$$

$$\langle P \rangle = \frac{1}{2} \left(\frac{3.3^2}{100} + \frac{3.3^2}{100} \right) = 100\text{mW}$$

 **Vtt termination consumes half the power as
Thevenin far end!**
*(another reason it is preferred- what is the
"cost"?)*



Power Consumed in RC

   


Voltage across capacitor "charges up"

Signal not centered @RX initially

$$\langle P \rangle = \frac{1}{2} \left(\frac{\Delta V_{lo}^2}{R} + \frac{\Delta V_{hi}^2}{R} \right)$$

 A few time constants later ~
50 x 10 nF ~ 1000 nsec





$$\langle P \rangle = \frac{1}{2} \left(\frac{\left(\frac{1}{2}3.3\right)^2}{50} + \frac{\left(\frac{1}{2}3.3\right)^2}{50} \right) = 50\text{mW}$$

Power consumed in RC termination is 1/2 as much as far-end single-resistor

Limitation with RC Termination

- Power dissipation advantage for 50% duty cycle
 - Less advantage with non 50% duty cycles
- Some data dependent jitter
 - Most suitable for clocks: with 50% duty cycle
 - Will have a turn on time for centered signal @RX
 - Might be ok for other data nets if jitter is acceptable (need to do PRBS simulation)

700 Mbps PRBS pattern

  

Lesson EPSI-03-80 Flyby Termination


Course EPSI: Essential Principles of Signal Integrity

With Eric Bogatin,
Signal Integrity Evangelist, Teledyne LeCroy Front Range Signal Integrity Lab
Dean, Teledyne LeCroy Signal Integrity Academy
Adjunct Professor, University of Colorado, Boulder, ECEE


- EPSI-03-80: recorded live, Dec 1, 2013
 - Where to place the terminating resistor
 - How to minimize the termination stub
 - Flyby termination
 - Limitations with RC terminations and why clocks are best

Which Termination to Use?


- Often times many “correct” answers
- If power is most important
 - source series termination
- If a clock net, lowest power, and minimum complexity:
 - RC termination
- If low duty cycle control line, mostly lo or mostly hi, lowest power if:
 - Far end termination to Vss or Vcc
- For reduced ground bounce @termination:
 - Provide connection to each plane used in the return path
- Good balance between: lower power, higher noise margin, higher bandwidth, but higher cost:
 - Far end Vtt termination
- ...but for the highest data rate:
 - It's the routing topology that sets the maximum supported data rate, not the termination strategy
 - You cannot “terminate away” reflections from poor routing topologies

 

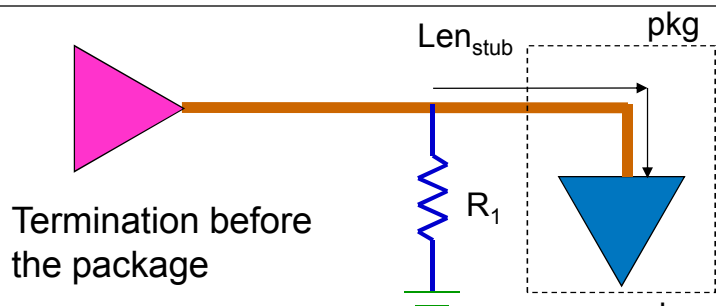Where Should the Far End Resistor Go? Does it Matter?




 Termination after the package:
“Fly-by” termination- enables shorter stubs






Which topology has shorter stub and higher BW?



 
Use the topology that enables the shortest termination stub length



   Termination Stub in Source Series Termination




   Place terminating resistor as close to Tx I/O pad as possible



Terminating BOTH the Differential and Common Signals

Tee termination topology

 

For differential signals

$$Z_{\text{diff}} = R_{\text{equiv}} = 2 R_1 = 2 \times Z_{\text{odd}}$$


$$R_1 = Z_{\text{odd}}$$

Common signals:

$$Z_{\text{comm}} = R_{\text{equiv}} = \frac{1}{2} R_1 + R_2 = \frac{1}{2} Z_{\text{even}}$$

Typical implementation: RC termination
 
$$R_2 = \frac{1}{2} (Z_{\text{even}} - Z_{\text{odd}})$$



$$R_1 = Z_{\text{odd}}$$

$$R_2 = \frac{1}{2} (Z_{\text{even}} - Z_{\text{odd}}) \sim 0$$


No DC power dissipation

Adds extra component to board- never ideal R, C

Difficult to do on die

C typically 1-100 nF

 Alternatively: Terminate as Single Ended Lines



Far end, Vtt termination of each line

Terminates both differential signal and common signal

Can be done on-die for shortest termination stub length



Rule #9: Never do a measurement or simulation without first anticipating what you expect to see.

If you are wrong, there is a reason- either the set up is wrong or your intuition is wrong. Either way, by exploring the difference, you will learn something

If you are right, you get a nice warm feeling that you understand what is going on.